

→ Decimal to Binary

÷ 2

→ Binary to Octal

÷ 8

→ Decimal to Hexadecimal

÷ 16

→ Binary to Octal
group of 3 bits

→ Binary to Hexadecimal
group of 4 bits

→ Octal to Binary
convert each to 3 bits

→ Octal to Hexa
→ binary

→ Octal to Decimal
multiply each digit
with power of 8

→ Hexadecimal to Octal
→ decimal

→ POSTULATES

Postulate 2 (a) $x+0=x$ (b) $x \cdot 1=x$

Postulate 5 (a) $x+x'=1$ (b) $x \cdot x'=0$

Theorem 1 (a) $x+x=x$ (b) $x \cdot x=x$

Theorem 2 (a) $x+1=1$ (b) $x \cdot 0=0$

Theorem 3, involution $(x')'=x$

Commutative (a) $x+y=y+x$ (b) $xy=yx$


Distributive (a) $x(y+z)=xy+xz$ (b) $x+yz=(x+y)(x+z)$

DeMorgan (a) $(x+y)'=x'y'$ (b) $(xy)'=x'+y'$


HALF ADDER




BINARY SUBTRACTOR

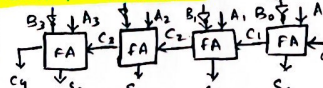


FULL ADDER

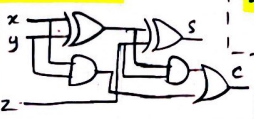

→ using 3x8 decoder

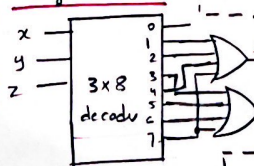


→ using MUX

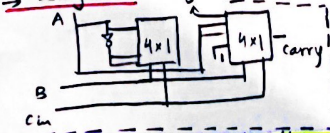


BINARY ADDER SUBTRACTOR

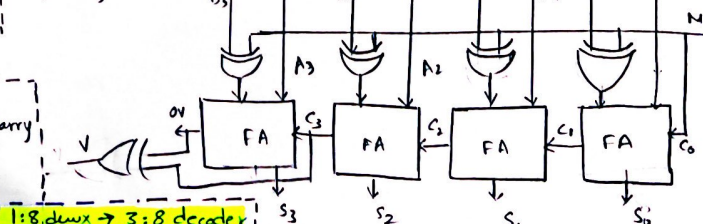→ if $V=0$, NO OVERFLOW
→ if $V=1$, OVERFLOW




1:4 Demux → 2:4 decoder // 1:8, demux → 3:8 decoder

→ Binary to Graycode

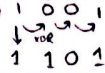

→ Graycode to Binary

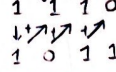

→ NAND Gate

→ NOR Gate

→ AND Gate

→ OR Gate

→ XOR Gate

→ XNOR Gate

→ Multiplexer

→ Demultiplexer

Minterm = 1 for Minterm $x=0, x'=1$

→ Converting function into sum of minterms / sum of product SOP

EXAMPLE: $A+B'C$

→ expand expression into sum of AND terms

→ check if each term has all variables;

$$A(B+B')(C+C') + B'C(A+A')$$

$$ABC + ABC' + AB'C + AB'C' + A'B'C \rightarrow \text{SOP form}$$

$$m_7, m_6, m_5, m_4, m_1$$

$$\Sigma (1, 4, 5, 6, 7) \rightarrow \text{canonical form}$$

→ Converting function into product of maxterms / POS

EXAMPLE: $xy+x'z$

→ converting into OR term using $A+BC=(A+BX)(A+CX)$ distributive law.

$$F = (x'+y)(x+z)(y+z)$$

→ check if each term has all variables.

$$(x'+y+z')(x+z+y')(y+z+xx')$$

$$F = (x+y+z)(x+y'+z)(x'+y+z) \rightarrow \text{POS form}$$


$$\Pi (0, 2, 4, 5) \rightarrow \text{canonical form}$$

Associative (a) $x+(y+z)=(x+y)+z$ (b) $x(yz)=(xy)z$

Absorption (a) $x+xy=x$ (b) $x(x+y)=x$

→ $A+A=A$
→ $A \cdot A=A$
→ $A \cdot (\bar{A} + B) = AB$


4-BIT ADDER

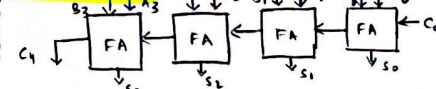

HALF SUBTRACTOR




HALF ADDER

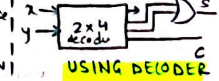


x	y	z	F
0	0	0	F=Z
0	0	1	F=Z'
0	1	0	F=Z'
0	1	1	F=Z
1	0	0	F=0
1	0	1	F=0
1	1	0	F=1
1	1	1	F=1


2x1 MUX

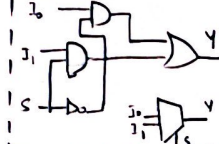

DECIMAL ADDER

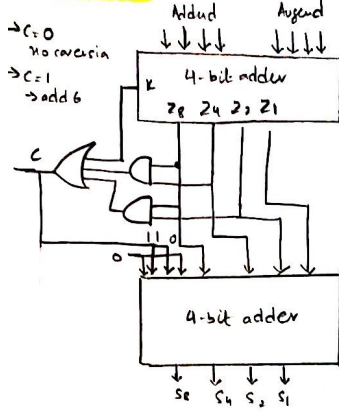


BCD-ADDER SUBTRACTOR

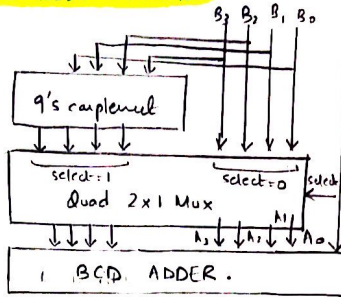

Mode = 0 for ADD
Mode = 1 for SUBTRACT


FULL SUBTRACTOR

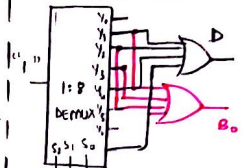


Gray-code to Excess 3-code

→ using 3x8 decoder.


5-BIT SUBTRACTOR

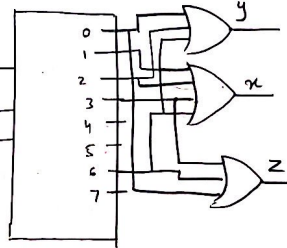

5-BIT SUBTRACTOR

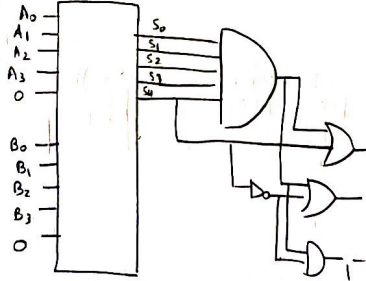


PRIORITY ENCODER

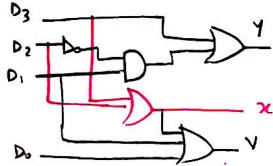

EQUALITY CHECKER

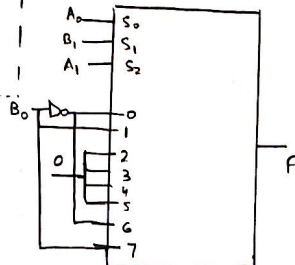→ using 8x1 MUX
 $A_1A_0 = B_1B_0$ (2 bit binary)
high when A=B



Decimal	2421	Gray code	EXCESS 3
0	0000	0000	0011
1	0001	0001	0100
2	0010	0011	0101
3	0011	0010	0110
4	0100	0100	1000
5	0101	0101	1001
6	1100	1101	1010
7	1101	1100	1011
8	1110	1111	